



Strathmore
UNIVERSITY

**SCHOOL OF COMPUTING AND ENGINEERING SCIENCES
BACHELOR OF SCIENCE IN ELECTRICAL AND ELECTRONIC ENGINEERING
END OF SEMESTER EXAMINATION**

BEE3203: ELECTRICAL MEASUREMENT AND INSTRUMENTATION

QUESTION PAPER

DATE: 19th December, 2023

Time: 10:30-12:30 Hours

Instructions

1. This examination consists of **FIVE** questions.
2. Answer **Question ONE (COMPULSORY)** and any other **TWO** questions.

QUESTION ONE

(Total: 30 Marks)

- a) Explain the meaning of the following terms as pertaining to taking of measurements:
 - i. Accuracy 1 mark
 - ii. Precision 1 mark
 - iii. Sensitivity 1 mark

- b) A basic D'arsenal movement with full scale deflection of $50\mu\text{A}$ and internal resistance of $1.8\text{k}\Omega$ is to be converted into a multirange dc voltmeter with voltage ranges of 0-1V, 0-10V, 0-30V and 0-250V
 - i. Design the multirange voltmeter 4 Marks
 - ii. Sketch the circuit arrangement of the DC voltmeter. 3 Marks

- c) In designing a measuring instrument, you are required to select a specific transducer. Explain in detail any five (5) selection criteria to consider in selecting a specific transducer. 5 Marks

- d) Figure 1 shows the Schematic diagram of a Wheatstone bridge with values of the bridge elements. The battery voltage is 5V and its internal resistance is negligible. The galvanometer has a current sensitivity of $10\text{mm}/\mu\text{A}$ and internal resistance of $100\ \Omega$. Calculate the deflection of the galvanometer caused by $5\ \Omega$ unbalanced in arm BC. 5 Marks

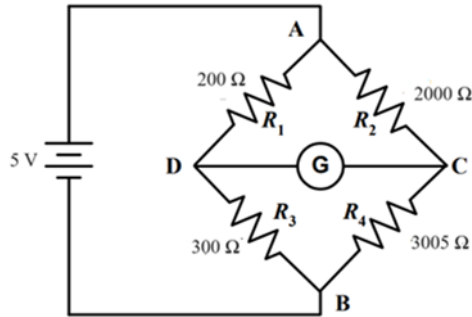


Figure 1

- e) Draw a generalized block diagram of data acquisition system and describe the function of each component. 5 Marks
- f) In a given laboratory session, you are required to obtain measurement of a signal magnitude and frequency.
- i. Mention the instrument to use and outline the procedure for obtaining the measurement 3 Marks
 - ii. Discuss the errors that might be associated with the instrument in question f(i) above. 2 Marks

QUESTION TWO

(Total: 15 Marks)

- a) Distinguish a standardization from calibration. 2 Marks
- b) Draw and describe the construction and working principle of single-phase induction type energy meter. 5 Marks
- c) A PMMC ammeter has the following specification; Coil dimension are 1cm x 1cm. spring constant is $0.15 \times 10^{-6} \text{ N-m/rad}$, flux density is $1.5 \times 10^{-3} \text{ wb/m}^2$. Determine the number turns required to produce a deflection of 900 when a current of 2 mA flows through the coil. 3 Marks
- d) Explain with neat diagram the working principle of LVDT. Give its applications. 5 Marks

QUESTION THREE


(Total: 15 Marks)

- a) State four characteristics of virtual instrumentation 2 Marks
- b) Explain the working principle of PMMC type equipment using torque equation. 6 Marks
- c) Describe the Hall-effect transducers with their application. 4 Marks
- d) With the help of neat sketch describe the method of measurement of earth resistance. 3 Marks

QUESTION FOUR

(Total: 15 Marks)

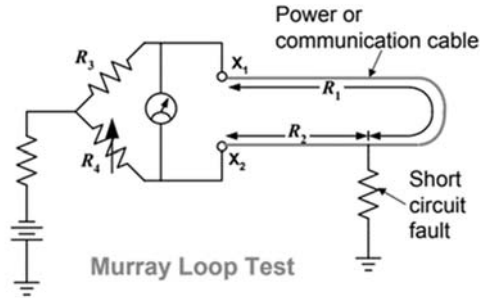- a) Explain the classification of analogue instruments and state one example of each
4 Marks
- b) Murray loop test is used to locate ground fault in a telephone system. The total resistance, $R = R_1 + R_2$ is measured by Wheatstone bridge, and its value is 300Ω . The conditions for Murray loop test are as follows: $R_3 = 1000 \Omega$ and $R_4 = 500 \Omega$. Find the location of the fault in meter, if the length per Ohm is 36.67 m .
5 Marks



- c) Explain the dual slope integrator digital voltmeters system with proper diagram and waveform.
6 Marks

QUESTION FIVE

(Total: 15 Marks)

- a) With the aid of a well labelled diagram, explain the operation of flash type ADC as used in measuring instruments.
5 Marks
- b) Explain the working principle of PMMC type equipment using torque equation.
5 Marks
- c) (i) Derive the equation for Maxwell bridge and solve a Maxwell inductance bridge uses a standard capacitor $C_3 = 0.1 \mu\text{F}$ and operate at a supply frequency of 100 Hz . Balance is achieved when $R_1 = 1.26 \text{ k}\Omega$, $R_3 = 470 \Omega$, and $R_4 = 500 \Omega$.
3 Marks
- (ii) Calculate the inductance and resistance of the measured inductor, and determine its Q factor.
2 Marks