



SCHOOL OF COMPUTING AND ENGINEERING SCIENCES
BACHALOR OF SCIENCE IN ELECTRICAL AND ELECTRONIC ENGINEERING
BSEE 3103 Unit Name: Network Theory
END OF SEMESTER EXAM

Date: 2nd December 2022

Time: Two Hours

Instructions:

This Examination consists of **FIVE** questions

Answer **Question ONE (COMPULSORY)** and any other **TWO** questions.

Question One [30 Marks]

- a) Write down the current and voltage relations (equations) for the following passive network elements. **(6 marks)**
- i. Resistance (R)
 - ii. Capacitance (C)
 - iii. Inductance (L)
- b) Consider a discrete LTI system with impulse response $h[n]$ and input signal $x[n]$, as illustrated in Fig. 1(b). Obtain and illustrate the output signal $y[n]$ for the system **(5 marks)**

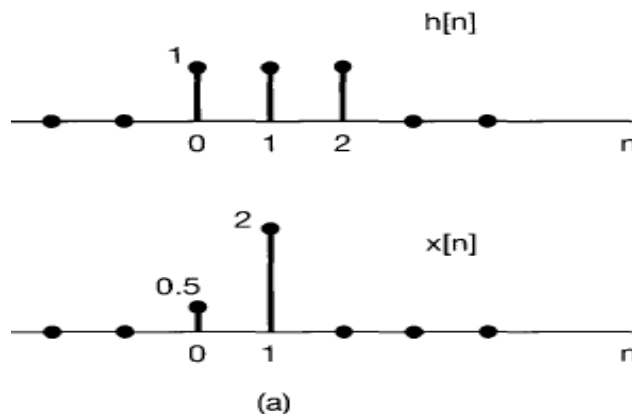


Fig. 1(b)

- c) Determine the transmission (ABCD) parameters in the s domain for the network shown Fig. 1(c) **(4 marks)**

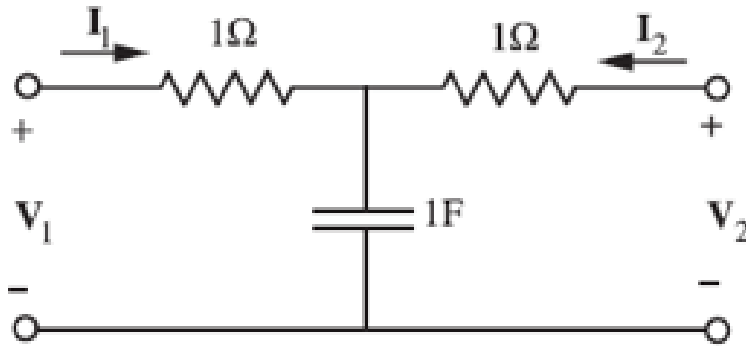


Fig. 1(c)

- d) For second order circuits (R-L-C), state and explain their classification, considering the damping factor (α) and resonant frequency (ω_0) **(5 marks)**
- e) Develop a Bode plot of a system whose mathematical model (response) is described by the transfer function **(6 marks)**

$$H(s) = \frac{1}{s+1} \Rightarrow H(j\omega) = \frac{1}{j\omega+1}$$

- f) Design a Butterworth Filter, to meet the following specifications/ requirements; **(4 marks)**
- No more than 1.5 dB deviation from ideal filter at 1300 Hz;
 - At least 35 dB for frequencies above 6000 Hz.

Question Two [15 Marks]

- a) Determine the h-parameters (expressed in terms of R_A , R_B , R_C and α) for the circuit shown in Fig. 2(b) **(7 marks)**

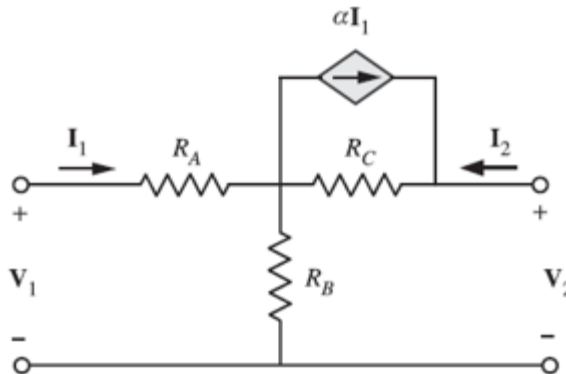


Fig. 2(b)

- b) Design a Chebyshev filter for the following specifications, using either bilinear transformation or impulse invariant method **(8 marks)**

Specifications

$$0.8 \leq |H(e^{j\omega})| \leq 1, \quad 0 \leq \omega \leq 0.2\pi$$

$$|H(e^{j\omega})| \leq 0.2, \quad 0.6\pi \leq \omega \leq \pi$$

Question Three [15 Marks]

a) Consider the electric circuit shown in Fig. 3(a).

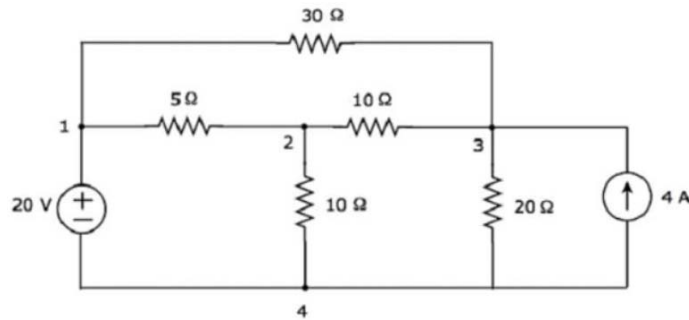


Fig. 3(a)

- i) State whether the network topology of this circuit is hinged or planar (1 mark)
 - ii) Develop the directed graph of the circuit (1 mark)
 - iii) From the directed graph in (ii) above, draw the tree and co-tree models of the circuit (2 marks)
 - iv) Obtain the cut-set matrix for the circuit (3 marks)
- b) The equivalent circuit of a short segment (Δz) of a two-wire transmission line is represented by a simple lumped-element equivalent circuit of Fig. 3(c). For this circuit, derive expressions for the propagation, phase and attenuation constants, as functions of the lumped parameters (R , L , G and C).

(8 marks)

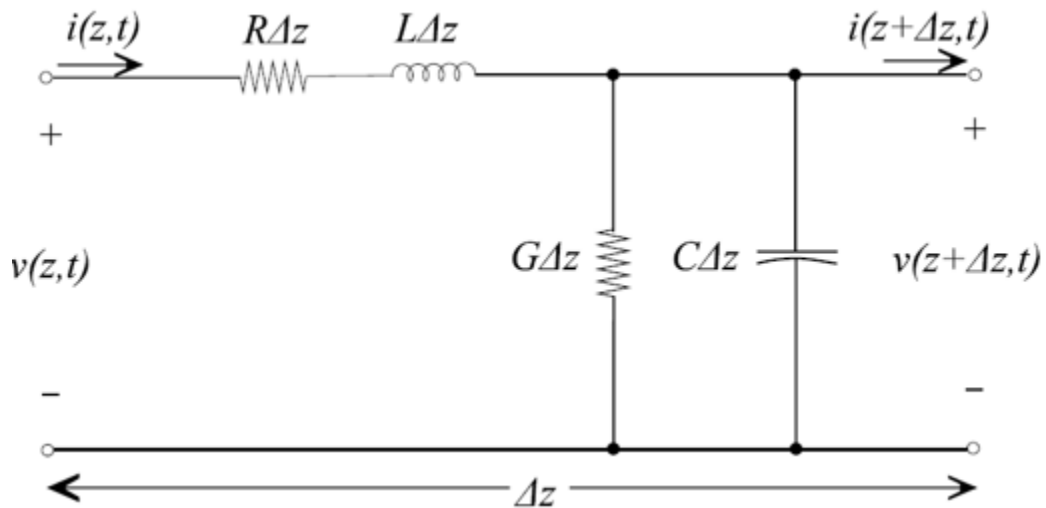


Fig. 3(c)

Question Four [15 Marks]

- a) In the parallel circuit of Fig. 4(b), find the natural response $v(t)$, for $t > 0$, assuming $v(0) = 5$ volts, $i(0) = 0$, $L = 1$ H, and $C = 10$ Mf. Consider a case where $R = 6.25$ Ohms. State if the system is classified as underdamped, critically damped or overdamped. **(7 marks)**

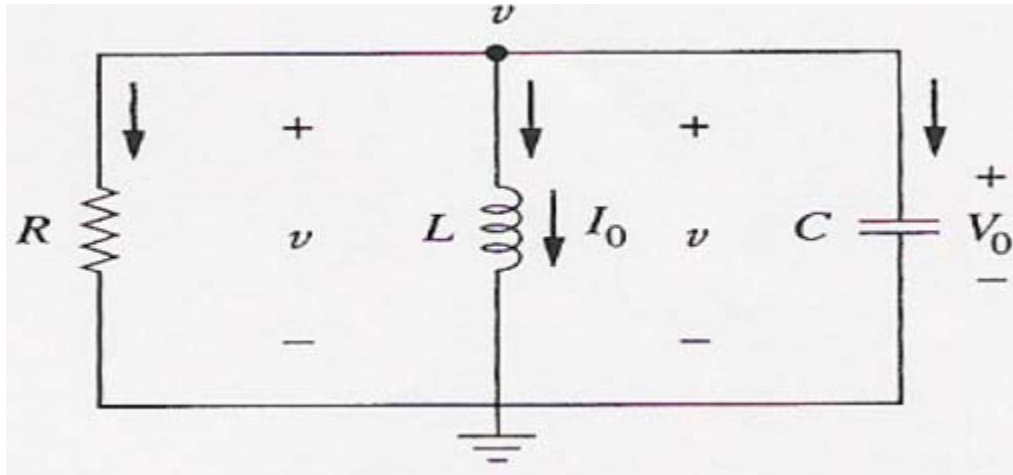


Fig. 4(b)

- b) Consider a satellite controlled by the PD controller whose feedback control model is shown in Fig. 4(c). Obtain the closed loop transfer function of this satellite controller and sketch its root locus **(8 marks)**

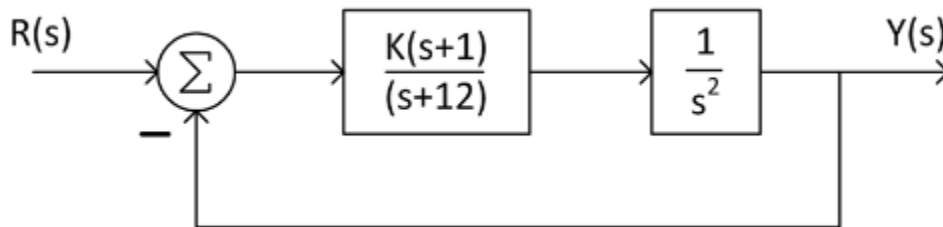


Fig. 4(c): PD Controller block diagram

Question Five (15 Marks)

- a) The characteristic equation of a system is given below. Determine the stability of the system by applying Routh Hurwitz Criteria and forming Routh array. **(3 marks)**

$$4s^4 + 8s^3 + 2s^2 + 10s + 3 = 0$$

- c) Synthesize the transfer function of the RC circuit shown in Fig. 3(b), state its poles (its stability limit) and represent the circuit in a block diagram **(6 marks)**

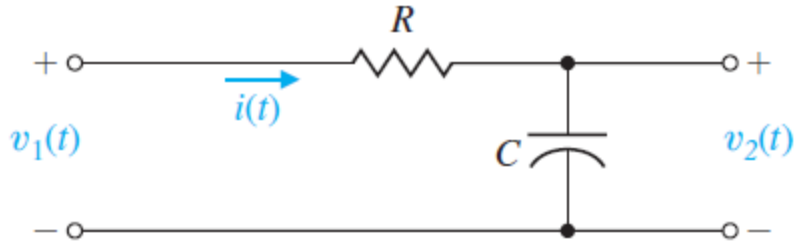


Fig. 3(b)

- c) Two identical 750 turn coils A and B lie in parallel planes. A current changing at the rate of 1500 A/s in coil A induces an e.m.f. of 11.25 V in coil B. Calculate the mutual inductance of the arrangement. If the self-inductance of each coil is 15 mH, calculate the flux produced in coil A per ampere and the percentage of this flux which links the turns of coil B.
(6 marks)

*****END*****

dB Scale Graph Paper

