

**SCHOOL OF COMPUTING AND ENGINEERING SCIENCES
BACHELOR OF ELECTRICAL AND ELECTRONICS ENGINEERING
END OF SEMESTER EXAMINATION**

BEE 3102: DIGITAL ELECTRONICS II

DATE: 28th October 2024

Time: 08:00 – 11:00

Instructions

1. This examination consists of **FIVE** questions.
2. Answer **Question ONE (COMPULSORY)** and any other **TWO** questions.
3. Do not write on the question paper.

QUESTION ONE

(Total: 30 Marks)

- a) A particular logic family has $V_{OH} = 5\text{ V}$, $V_{OL} = 1\text{ V}$, $V_{IH} = 3.5\text{ V}$, and $V_{IL} = 2\text{ V}$. Determine its noise margin NM_H and NM_L . (4 Marks)
- b) Develop the truth tables for the logic families' circuits in figure 1 and state their respective logic families. (4 Marks)

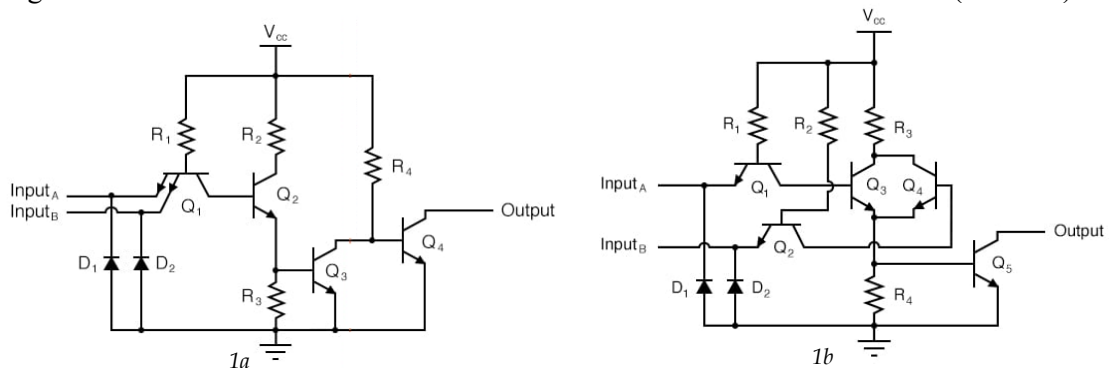


Figure 1

- c) Using clearly labelled block diagrams, differentiate between Programmable Read Only Memory (PROM), Programmable Array Logic (PAL), and Programmable Logic Array (PLA). (3 Marks)
- d) What is the sequence detected by the sequence detector in figure 2? (3 Marks)

 


Figure 2

- e) A 16-bit Digital-to-Analog Converter (DAC) using a Binary Coded Decimal (BCD) input code has a full-scale output of 9.99V. Calculate the percentage resolution and the output voltage (V_{out}) for an input code of 0110100101010111. (3 Marks)
- f) A given sequential network has one input and one output. The output becomes 1 and remains 1 thereafter when at least two zeros and at least two ones have occurred as inputs, regardless of the order of occurrence. Draw a state graph (Moore type) for the network. *Note: 9 states are sufficient and your final state graph should be neatly drawn with no crossed lines.* (4 Marks)
- g) A 6-bit D/A converter produces an output voltage of 12 V for an input code of 101010. What will be the value of the output voltage for an input code of 110110? (3 Marks)
- h) Illustrate with block diagrams and discuss the following terms as used in Algorithmic State Machines
- State Box (2 Marks)
 - Decision Box (2 Marks)
 - Combinational Box (2 Marks)

QUESTION TWO

(Total: 15 Marks)

- a) Realize a PROM using the following expression. (5 Marks)

$$(a, b, c) = \sum m(0, 1, 3, 5, 7) \text{ and } f_2(a, b, c) = \sum m(1, 2, 5, 6)$$
- b) Design a 4-bit DAC using binary-weighted resistors and calculate the output voltage for an input code of 1101, given that the reference voltage is 5V. (6 Marks)
- i) Draw a clearly labelled schematic diagram for a 2 input CMOS NAND gate. (4 Marks)

QUESTION THREE

(Total: 15 Marks)

- a) Design an overlapping sequence detector to detect 1001 from a data sequence of 100100100100111011 by answering the following questions
- Draw a state diagram for this detection. (3 Marks)
 - Develop a corresponding state table and perform the state assignment (2 Marks)
 - Using JK flip flops, draw the excitation table (4 Marks)
 - Using K-Maps, minimize the functions of output and flip flop inputs (3 Marks)
 - Draw the circuit diagram using block Diagram of JK flip flops and basic gates (3 Marks)

QUESTION FOUR

(Total: 15 Marks)

- a) Reduce the number of states in state diagram in Figure 2 using;
 - i. Partitioning method (4 Marks)
 - ii. Implication Tables method (4 Marks)

 


Figure 2

- b) Draw a block diagram of Mealy and Moore machines and discuss their differences (4 Marks)
- c) Illustrate and discuss the concept of memory decoding (3 Marks)

QUESTION FIVE

(Total: 15 Marks)

- a) A 3-bit Flash ADC is used to digitize an analog input signal. Given a reference voltage V_{REF} is 8V;
 - i. Determine the number of comparators required for this Flash ADC. (2 Marks)
 - ii. Calculate the voltage resolution of the ADC. (2 Marks)
 - iii. Determine the digital output for an analog input voltage of 5.5, 5.8, 3.8, and 4.6 V. (6 Marks)
- b) Write a Verilog program for a Full Adder. (5 Marks)