



SCHOOL OF COMPUTING AND ENGINEERING SCIENCES
BACHELOR OF SCIENCE IN ELECTRICAL AND ELECTRONIC ENGINEERING
BEE 2201: DIGITAL ELECTRONICS I
END OF SEMESTER EXAM

Date: 13th March, 2025

Time: 08.30 - 11.30

Instructions:

1. This Examination consists of **FIVE** questions
 2. Answer **Question ONE (COMPULSORY)** and any other **TWO** questions.
-

Question 1

- a. Convert the following values to their respective forms. (5marks)
 - i. 1100.625_{10} to binary
 - ii. $3FEE.1CC_{16}$ to decimal
 - iii. 1110010.0011_2 to decimal
 - iv. 177_{10} to Octal
 - v. 110.567_{16} to BCD
- b. Draw the truth table for a half subtractor and the circuit diagram from the truth table (4marks)
- c. Realize a JK flipflop using the SR flipflop (Draw the truth table and the circuit diagram) (4marks)
- d. Implement the following circuit using NOR and NAND gates (4marks)
$$x = (A + B)(B + C)(A + C)$$
- e. Subtract $(1110.011)_2$ from $(11011.11)_2$ using basic rules of binary subtraction and verify the result by showing equivalent decimal subtraction. (5 marks)
- f. Simplify the following expression $F(A, B, C, D) = \sum m(1,3,4,5,6,7,9,12,13)$ (4marks)
- g. Draw the circuit diagram for a Static RAM and explain the working of the circuit. (4marks)

Question 2

Given figure 1 below of a 7-segment decoder, answer the following questions.

 


Figure 1

- Draw the truth table for conversion from binary 0-9 (4marks)
- Draw the K-maps for all the segments (8marks)
- Draw the circuit diagram for the 7-segment decoder (3marks)

Question 3

- State the differences between synchronous and asynchronous sequential circuits (2marks)
- Draw the circuit diagram and function table for a SR Latch with control input using NAND gates, and explain its working (6marks)
- Given the figure 2 below answer the following questions.

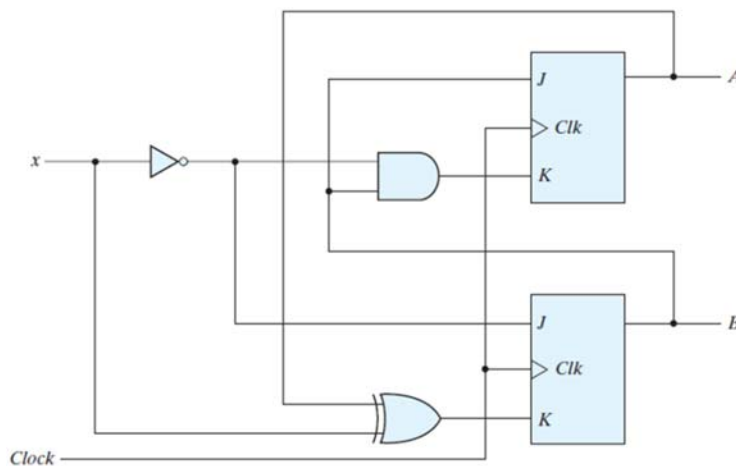


Figure 2

- i. Derive the input equations to each flipflop (2marks)
- ii. Draw the state table for the above sequential circuit (3marks)
- iii. Draw the state diagram for the above sequential circuit (2marks)

Question 4

- a. Figure 3 below shows a 4-bit in serial out shift register that is shifted from left. Assuming that the register is initially clear, develop a state table to clearly show the 4-bit pattern after the third clock pulse if we wish to store the nibble 1100. (2marks)

 


Figure 3

- b. Give the differences between a synchronous counter and a ripple counter (4marks)
- c. For a 3bit ripple counter using JK flipflops, draw the circuit diagram, truth table and the timing diagram to explain its functionality (9marks)

Question 5

- a. Explain the different types of ROMs (3marks)
- b. Using diagrams discuss the following types of programmable Logic Configurations.
 - i. PROM (2marks)
 - ii. PAL (2marks)
 - iii. PLA (2marks)
- c. Using the following truth table, design a ROM to show address line 3 using a fuse link (3marks)

ROM Truth Table (Partial)

Inputs					Outputs							
I_4	I_3	I_2	I_1	I_0	A_7	A_6	A_5	A_4	A_3	A_2	A_1	A_0
0	0	0	0	0	1	0	1	1	0	1	1	0
0	0	0	0	1	0	0	0	1	1	1	0	1
0	0	0	1	0	1	1	0	0	0	1	0	1
0	0	0	1	1	1	0	1	1	0	0	1	0
		⋮							⋮			
1	1	1	0	0	0	0	0	0	1	0	0	1
1	1	1	0	1	1	1	1	0	0	0	1	0
1	1	1	1	0	0	1	0	0	1	0	1	0
1	1	1	1	1	0	0	1	1	0	0	1	1

- d. Design a counter system with three inputs denoted A, B, C. Presence or absence of an input is represented by 1 and 0 respectively and the output is a two-bit number X_1X_0 , representing that count in binary. (3marks)
- Write the truth table for this circuit.
 - Find the minimized logic equations for outputs X_1 and X_0 ;
 - Draw the corresponding labelled logic diagram for this circuit using basic gates