



SCHOOL OF COMPUTING AND ENGINEERING SCIENCES
BACHELOR OF SCIENCE IN ELECTRICAL AND ELECTRONIC ENGINEERING
BEE 3205: ANALOGUE ELECTRONICS II
END OF SEMESTER EXAMINATIONS

Date: 17th March 2025.

Time: 11:00-13:30 Hours

Instructions:

1. This Examination consists of **FIVE QUESTIONS**
2. Answer **Question ONE (COMPULSORY)** and any other **TWO** questions.

QUESTION ONE

- a) State **two** causes of distortions in class B amplifiers and their **possibly remedies** (2 marks)
- b) State **TWO** characteristics of an ideal operational amplifier (2 marks)
- c) Figure 1 shows an operational amplifier circuit. State **THREE** characteristics of the circuit and explain the use of the circuit. (4 marks)


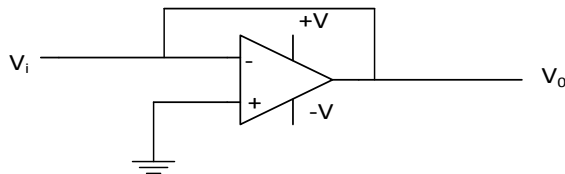


Figure 1

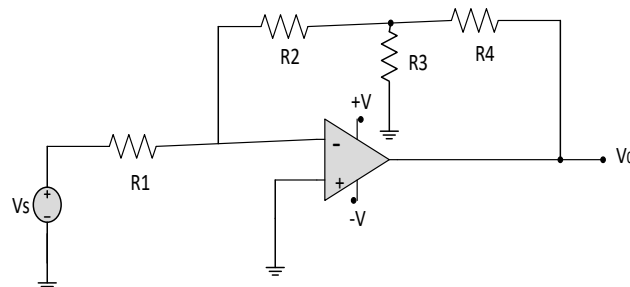- d) Explain the significance of slew rate in the performance of operational amplifiers (2 marks)
- e) Figure 2 shows an operational amplifier circuit. Obtain the closed loop gain of the circuit, $A = V_0/V_s$ (4 marks)



(4 marks)

- f) Draw the basic circuit diagram of that performs the following operations
- Integrator
 - Differentiator
 - Anti-logarithmic function
- (6 marks)
- g) Explain the significance of gain-bandwidth product in operational amplifiers
- (2 marks)
- h) State the Barkhausen criteria of oscillation in oscillators
- (2 marks)
- i) Figure 2 shows an op-amp based RC oscillator. Determine each of the following:
- Feedback factor β ;
 - Magnitude of the loop gain $T(s) = A_{CL}\beta$;
 - Frequency of oscillation f_o .
- (6 marks)

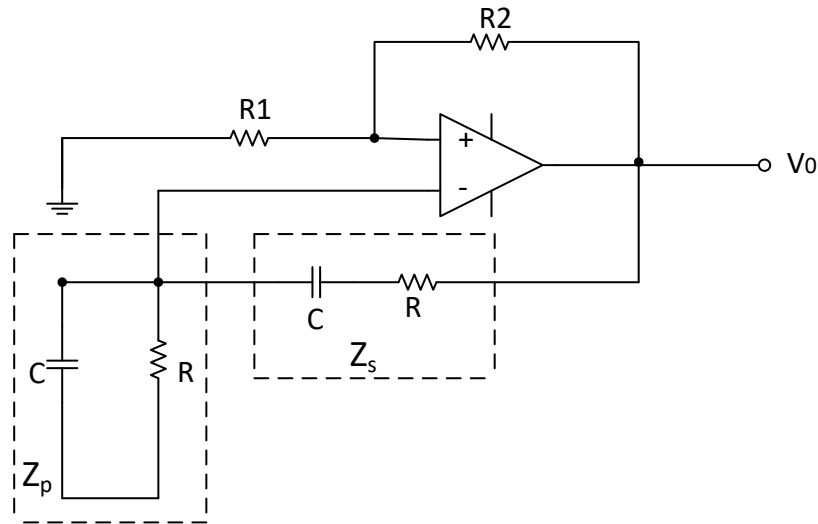


Figure 2

QUESTION TWO

- a) Figure 2 shows a class A power amplifier.
- Determine the following d.c values
 - Emitter current I_E
 - The dc collector voltage, V_C
 - The collector emitter voltage, V_{CEQ}
 - The transistor power dissipation P_{DC}

(8 marks)
 - The efficiency of the amplifier given that the peak output voltage is 18V
- (5 marks)

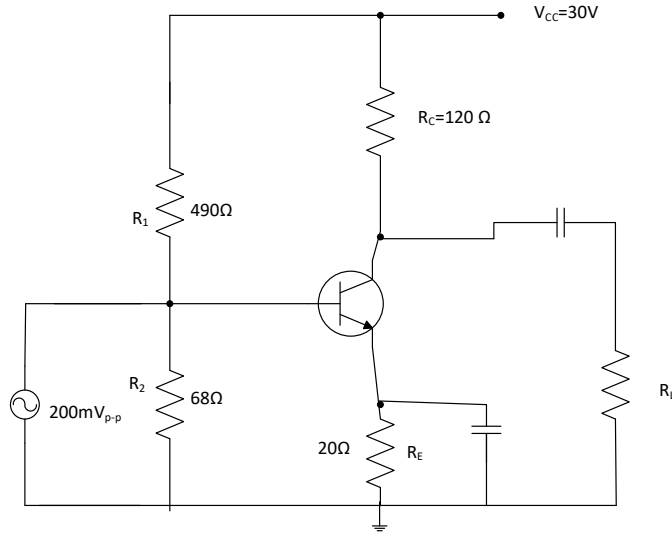


Figure 3

b) State one advantage and one disadvantage of a class A amplifier

(2 marks)

QUESTION THREE

a) Figure 3 shows a simplified block diagram of an operational amplifier. Identify the circuit configurations in block A and B and state why they are suitable for the functions performed by the blocks

(4 marks)

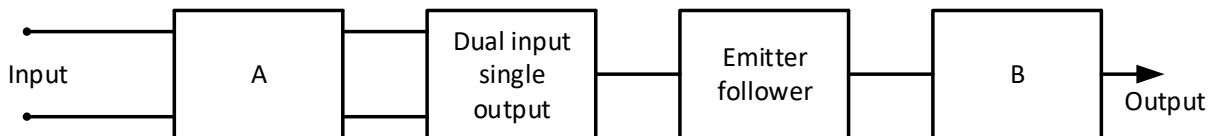


Figure 4

b) Identify the configuration of the differential amplifier shown in Figure 4

(1 mark)

c) Perform the dc analysis and obtain the:

- i. Tail current, I_T
- ii. Emitter current, I_E
- iii. Quiescent collector emitter voltage, V_{CEQ}

(6 marks)

d) Given that for both transistors, $\beta = 300$ obtain the:

- i. ac output voltage;
- ii. input impedance of the differential amplifier.

(4 marks)

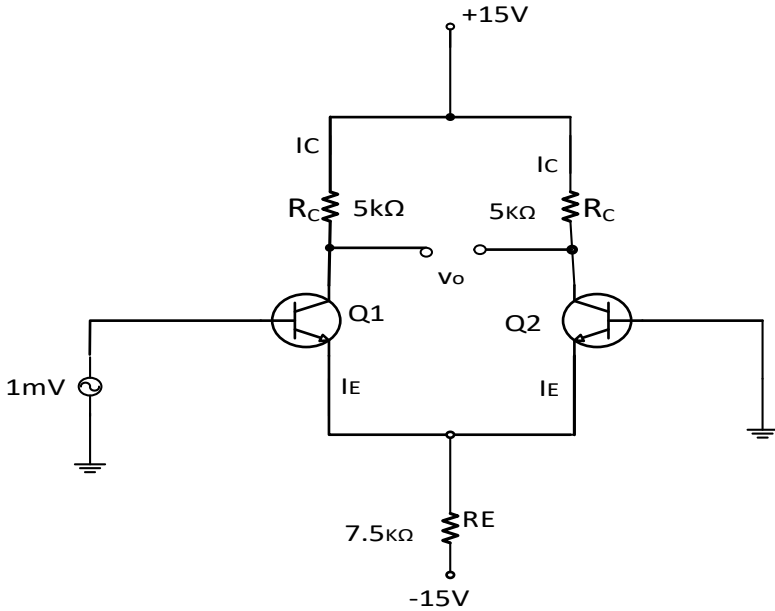


Figure 5

QUESTION FOUR

- a) The amplifier in Fig. 5 has an open gain equal to -2500 and open loop output resistance of 100Ω . Determine the:
- i. Magnitude of the open loop gain (2 marks)
 - ii. Closed loop gain (2 marks)
 - iii. Input resistance r_{if} see by V_{in} (2 marks)
 - iv. The closed loop output resistance r_{of} (2 marks)


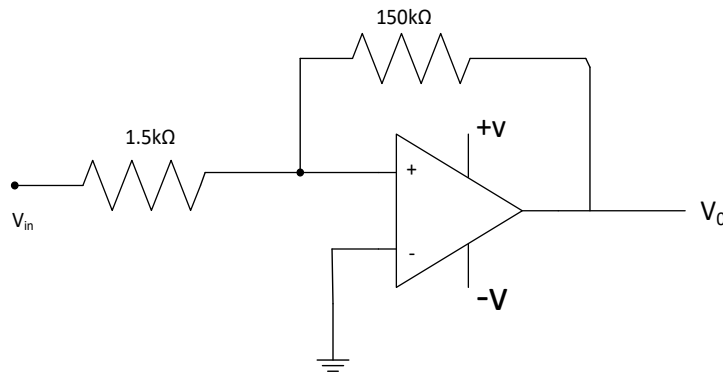


Figure 6

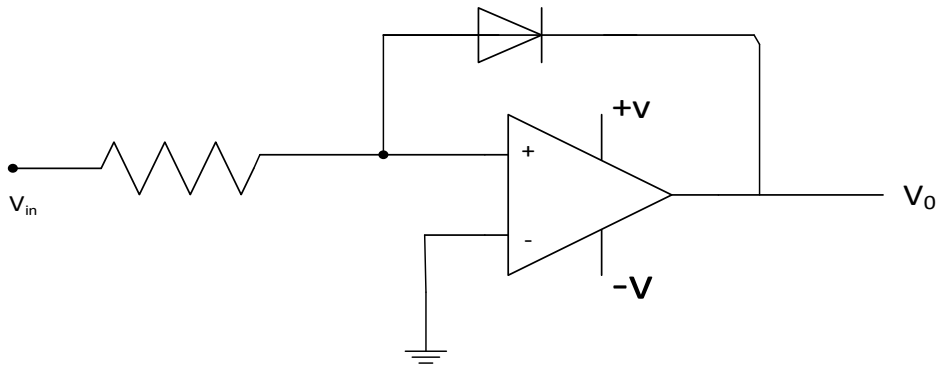- b) Explain two areas of application of logarithmic amplifiers (2 marks)
- c) Figure 6 is a logarithmic amplifier. Derive the output expression of the amplifier (5 marks)



QUESTION FIVE

a) Figure 7 shows an application of a comparator to control street light.

(6 marks)


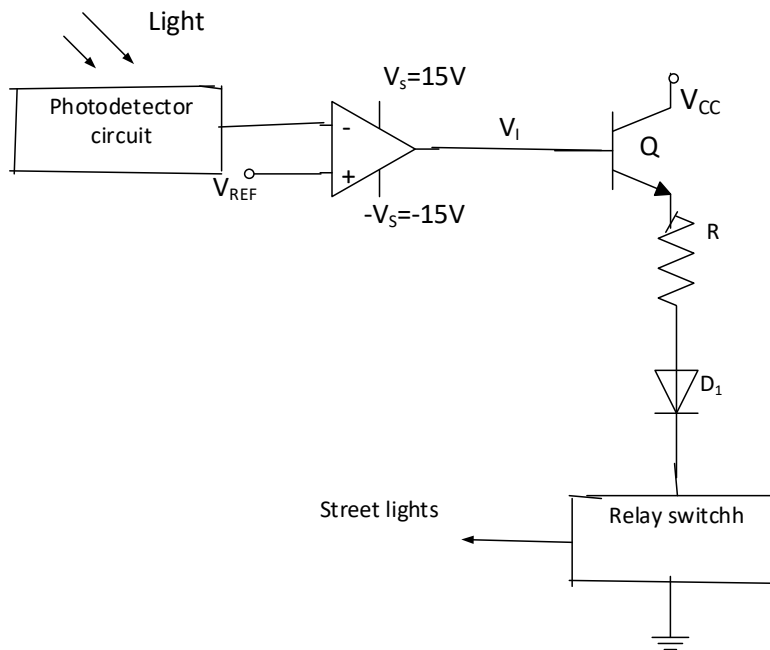


Figure 7

b) Figure 1 shows a circuit diagram of a monostable multivibrator using 555 timer IC. The supply voltage is +12 volts. Resistor values are $R_1 = 71.0 \text{ k}\Omega$ $R_2 = 15.0 \text{ k}\Omega$.

- i. Determine the value of the capacitor C_1 that should be used to obtain a pulse width of 2.0 s at the output of a monostable multivibrator.

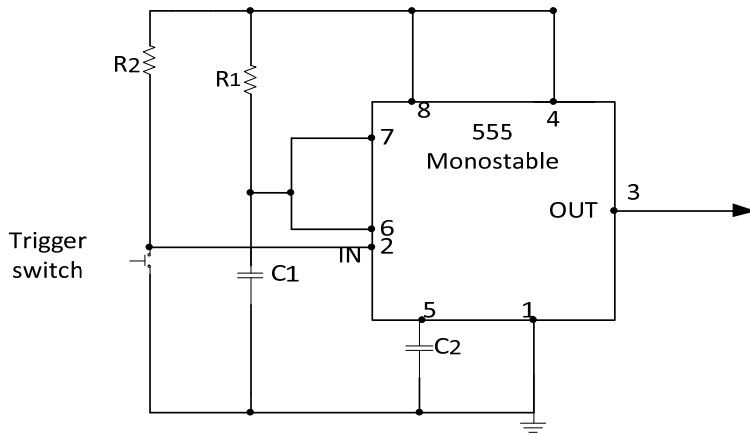- i. Explain the reason for the use of resistor R_2 in the circuit and capacitor C_2 (6 marks)



- c) Explain possible areas of application of the current to voltage converters (3 marks)

(3 marks)