



School of Computing and Engineering Sciences

Bachelor of Science in Electrical and Electronics Engineering

End of Semester Examination

BEE2201: Digital Electronics I

Date: 6TH March 2024

Time 08:00-11:00 Hours

Instructions: Answer Question **ONE** and any other **TWO** Questions

Question ONE (30 Marks)

- a) Convert the following to the base indicated
- i. $(1001.0101)_2$ to decimal 1 Marks
 - ii. $(13.375)_{10}$ to binary 1 Marks
 - iii. $(73.75)_{10}$ to Octal 1 Marks
 - iv. $(762.013)_8$ to Hexadecimal 1 Marks
- b) Perform the following operation using 2's complement method
- i. $(37)_{10} + (-18)_{10}$ (2 Marks)
 - ii. Subtract $(-64)_{10}$ from $(32)_{10}$ (2 Marks)
- c) Simplify the following Boolean expression using Boolean laws
- i. $Y = AB + A'B + AB' + (AB)'$ (2 Marks)
 - ii. $X = A' + ABC + A(B \oplus C) + AB'C'$ (2 Marks)

- d) Obtain the minterm expansion for $F(A,B,C)$ in fig.1 below (2 Marks)

 


Fig. 1

- e) For a given Boolean function $F(A,B,C,D)=\sum(0,2,5,7,10,13,15)$ which has don't care conditions $d(A,B,C,D)=\sum(4,8,14)$.

- i. Simplified the Boolean function using Karnaugh Map. (2 Marks)
 - ii. Implement F with only NAND gates (2 Marks)
- f) Implement a full adder circuit using 3 to 8-line decoder. (4 Marks)
- g) The 100kHz square waveform of fig 2(a) below is applied to the clocked input of the flip-flop shown in fig 2(b). If the Q output is initially '0',
- i. Draw the output Q waveform. (1 Mark)
 - ii. Determine the frequency of the Q output (1 Mark)

 
 


Fig. 2


- h) Show how to implement two input OR gate using NOR gates (2 Marks)
- i) Draw the logic diagram of a 4-bit serial in serial out shift register using JK flip-flops and explain its working with an example. (4 Marks)

Question TWO (15 Marks)

- a) A 4-bit binary number is applied to a circuit on four lines A, B, C, and D. the circuit has a single output, F, which is true if the number is in the range of four to eleven, inclusive.
- i. Draw a truth table to represent the problem (3 Marks)
 - ii. Use the K-map to obtain a simplified expression for the function (3 Marks)
 - iii. Construct a circuit to implement the simplified expression in (ii) above using NAND gates only (3 Marks)
- b) Briefly explain the following terms: -
- i. Registers (1 Mark)
 - ii. Shift-registers (1 Mark)
- c) With the aid of logic symbols and truth tables, explain the operation of the following two-input gates.
- i. NOR (2 Marks)
 - ii. XOR (2 Marks)

Question THREE (15 Marks)

- a) Analyze the following circuit


 


- i. Obtain the Boolean expression for the output (F) (4 Marks)
- ii. Use the truth table and determine the output F as sum of minterms and product of maxterms (4 Marks)
- iii. Use Karnaugh Map to simplify the equation obtained in (i). (3 Marks)
- iv. Implement the SOP and POS circuits with minimum number of gates. (4 Marks)

Question FOUR (15 Marks)

- a) Design a combinational circuit that accepts a four bit number (A,B,C,D) and generates an output which is equal to the sum of the binary numbers formed by the input (AB) and (CD). (10 Marks)

  - b) Complete the given timing diagram for the circuit shown below (5 Marks)



Question FIVE (15 Marks)

- a) The logic diagram of Fig. 1 performs the function of a very common arithmetic building block. Identify the logic function. (5 Marks)

 


Fig. 1

- b) Design modulus 12 asynchronous counter with a straight binary sequence from 0000 through 1011 using J-K flops. Draw the circuit diagram and associated timing diagram. (10 Marks)