



Strathmore  
UNIVERSITY

SCHOOL OF COMPUTING AND ENGINEERING SCIENCES  
BACHELOR OF SCIENCE IN ELECTRICAL AND ELECTRONICS ENGINEERING  
2<sup>nd</sup> SEMESTER 2023/2024 - UNIVERSITY EXAMINATION  
BEE 1201: CIRCUIT THEORY I

DATE: 11<sup>th</sup> March, 2024

Time: 15:30pm – 17.30pm

**Instructions**

1. This examination consists of **FOUR** questions.
2. Answer **QUESTION ONE** and any other **TWO QUESTIONS**.

**Question 1 (30 Marks)**

Q1(a) Given the circuit shown in Fig. Q1(a), use source transformations to find  $I_x$

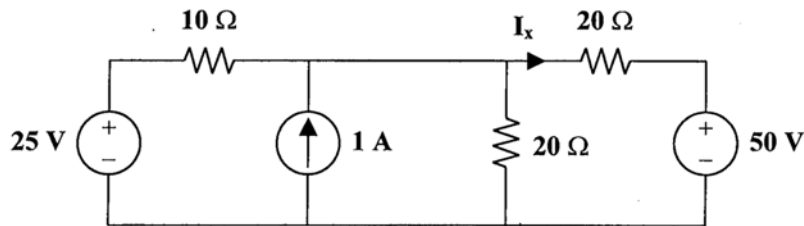


Fig. Q1(a)

6 Marks

(b) For the circuit shown in Fig. Q1(b), assuming an ideal op-amp, find  $v_o$  and  $i_o$

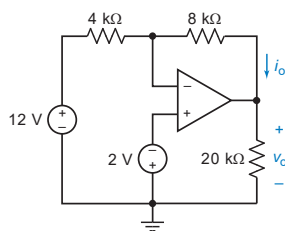


Fig. Q1(b)

6 Marks

(c) The circuit shown in Fig. Q1(c) is at steady state before the switch closes at time  $t = 0$ . Determine the capacitor voltage,  $v(t)$ , for  $t \geq 0$ .

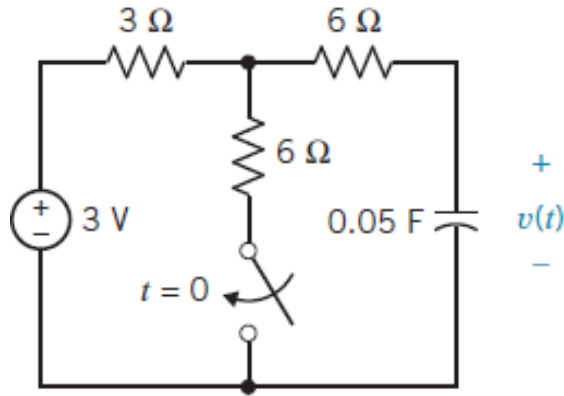


Fig. Q1(c)

6 Marks

(d) Given the circuit shown in Fig. Q1(d) where  $i_s(t) = 10\cos(1000t)$ , assuming steady state values, find  $v_s(t)$  and  $v_c(t)$

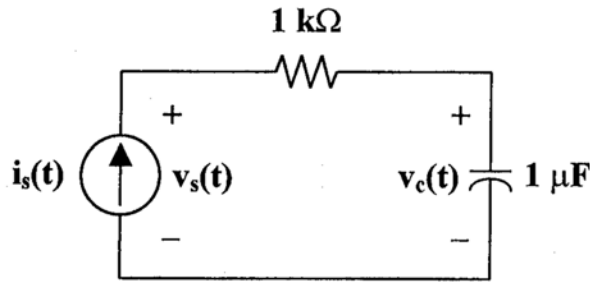


Fig. Q1(d)

6 Marks

(e) A relay coil circuit shown in Fig. Q1(e) is connected to a 240V, 50Hz mains supply, calculate

- (i) power consumed by the  $30\Omega$  resistor 2 Marks
- (ii) apparent power supplied by the source and 2 Marks
- (iii) the power factor. 2 Marks

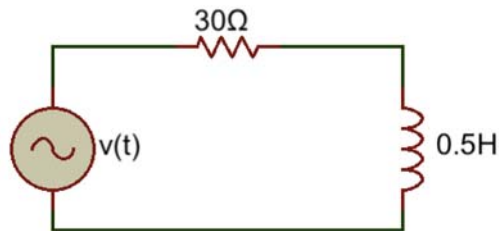


Fig. Q1(e)

**Question 2 (15 Marks)**

(a) Find the Norton equivalent circuit for the circuit shown in Fig. Q2(a)

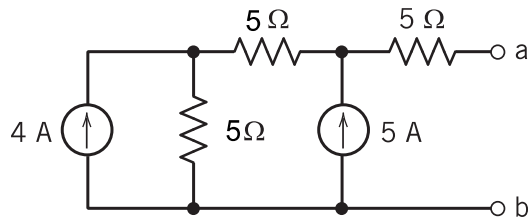


Fig. Q2(a)

5 Marks

(b) Given the circuit shown in Fig. Q2(b), use **mesh analysis** to find  $V_x$

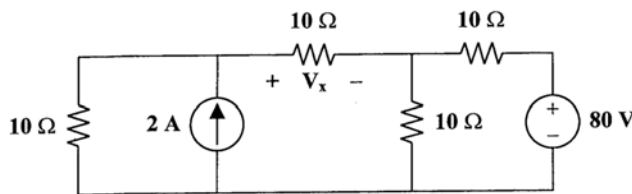


Fig. Q2(b)

10 Marks

**Question 3 (15 Marks)**

(a) For the circuit shown in Fig. Q3(a);

- (i) find the value of source resistance and
- (ii) load resistance  $R_L$  that will result in maximum power transfer.
- (iii) For the value of  $R_L$  calculated in (ii) find the maximum power transferred.

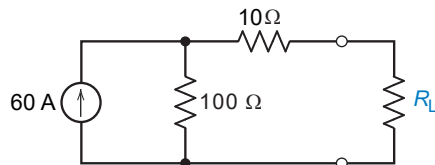


Fig. Q3(a)

5 Marks

(b) Use **nodal analysis** to find  $I_x$  in the circuit shown in Fig. Q3(b)

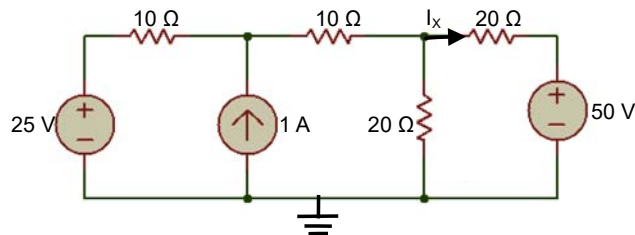


Fig. Q3(b)

10 Marks

**Question 4 (15 Marks)**

- (a) Fig. Q4(a) shows an unbalanced wye connected resistors supplied from a balanced wye connected 3 phase source having 415.69V line to line voltage. Calculate the power delivered to each resistor.

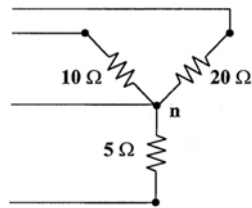


Fig. Q4(a)

3 Marks

- (b) Given the circuit shown in Fig. Q4(b) where  $v_i(t) = 10\cos(1000t)$ , find  $v_o(t)$ .

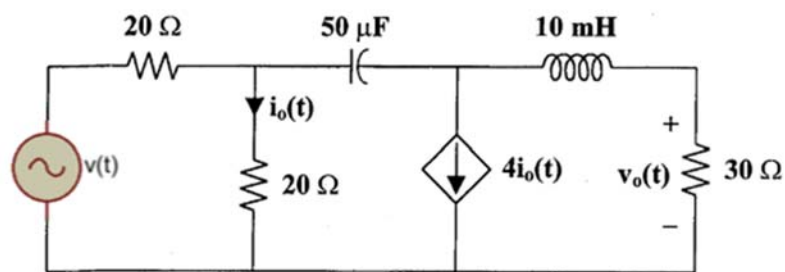


Fig. Q4(b)

12 Marks