



Strathmore
UNIVERSITY

SCHOOL OF COMPUTING AND ENGINEERING SCIENCES
BACHELOR OF SCIENCE IN ELECTRICAL AND ELECTRONIC ENGINEERING
END OF SEMESTER EXAMINATION
BEE3205 ANALOGUE ELECTRONICS II

DATE: 11th December 2023

Time: 08:00-11:00 Hours

Instructions

1. This examination consists of **FIVE** questions.
2. Answer **Question ONE (COMPULSORY)** and any other **TWO** questions.

QUESTION 1 (30 marks)

- a) State the **criterion** for the classification of power amplifiers (1 marks)
- b) State the Barkhausen criterion of oscillation in oscillators (2 marks)
- c) Figure 1 shows a circuit diagram of a monostable multivibrator using 555 timer IC. The supply voltage is +12 volts. Resistor values are $R_1 = 71.0\text{ k}\Omega$ $R_2 = 15.0\text{ k}\Omega$.
 - i. Determine the value of the capacitor C_1 that should be used to obtain a pulse width of 2.0 s at the output of a monostable multivibrator.
 - ii. Explain the reason for the use of resistor R_2 in the circuit and capacitor C_2 (5 marks)

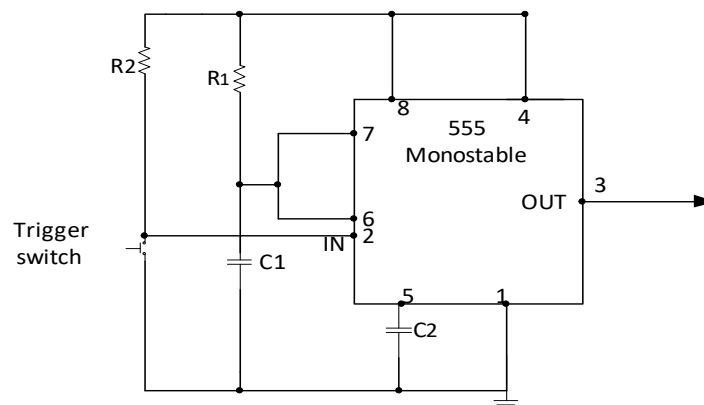


Figure 1

- d) Explain the:

- i. origin of the **two** distortions in class B amplifiers;
- ii. solutions to the problems in c(i).

(4 marks)

e) The block diagram in Fig.2 shows the main circuit components of an operational amplifier.

- i. Name the blocks A and B.
- ii. State the reasons for the circuit components used in the input and output.

(4 marks)

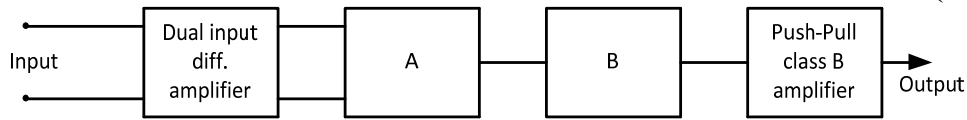


Figure 2

g) An ideal op-amp voltage inverting amplifier is shown in Fig. 3 with ideal input impedance R_i and voltage gain A_v .

- i. Derive the expression of Z_i
- ii. show that if Z is:

- I. a capacitor, then the Miller capacitance is given by $C_m = C(1 + A_v)$
- II. a resistor R then the input impedance $Z_i \approx R_i$

(6 marks)

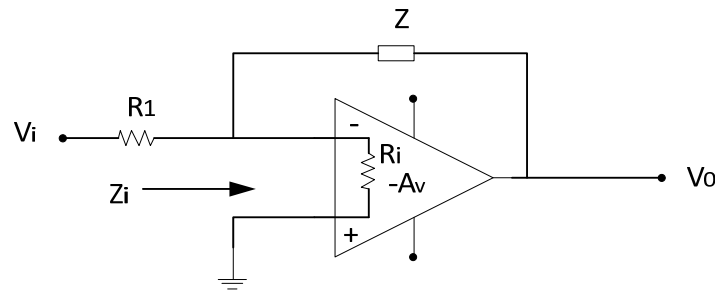


Figure 3

f) Explain the significance of **gain-bandwidth** product in operational amplifiers

(2 marks)

g) State the **three** classifications of the multivibrators

(3 marks)

h) Draw the diagram of a **voltage follower** amplifier and state its area of application.

(3 marks)

QUESTION TWO

a) State **Two** features of a differential amplifier

b) For the amplifier in Fig.4

i. Perform the dc analysis and obtain the:

- I. Tail current, I_T
- II. Emitter current, I_E
- III. Quiescent collector emitter voltage, V_{CEQ}

ii. Given that for both transistors, $\beta = 300$ obtain the:

- I. ac output voltage;
- II. input impedance of the differential amplifier.

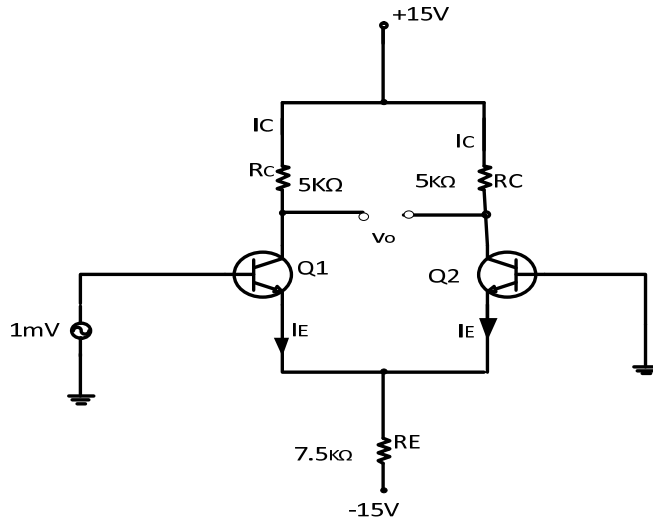


Figure 4

- c) Figure 5 shows an op amp differential circuit. Derive the expression for the output voltage V_0 .

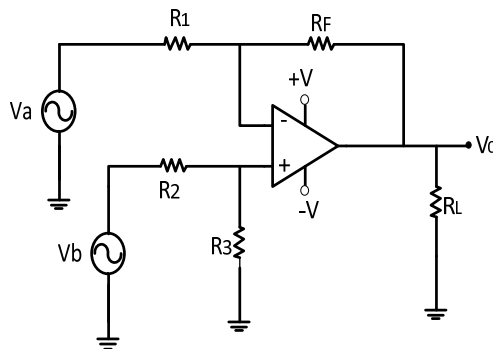


Figure 5

QUESTION THREE

- a) Figure 6 shows a class C tuned circuit.
- i. Identify the clamper bias circuit and explain its usage in the amplifier operation.
 - ii. With reasons, state the possible areas of application of the amplifier.
- b) For the components values in given in Fig. 6, determine each of the following:
- i. The resonance frequency;
 - ii. The equivalent parallel resistance of the coil R_p given that the Q_L of the inductor is 100
 - iii. The Q-factor of the overall circuit;
 - iv. The bandwidth of the circuit;

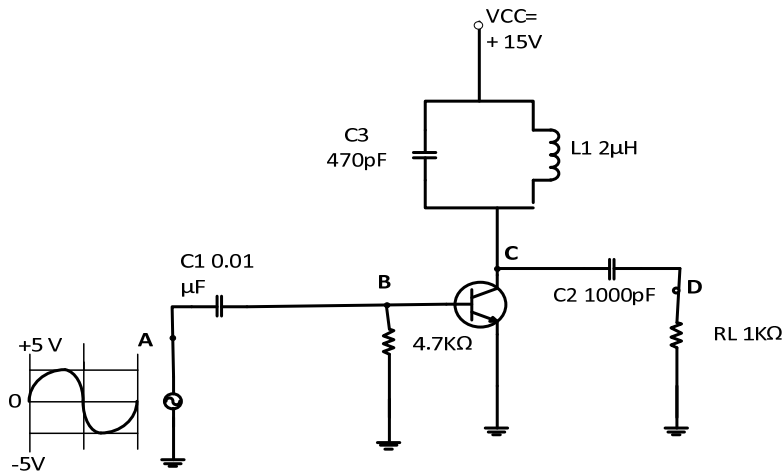


Figure 6

- c) Figure 7 shows a class B push-pull configuration amplifier. Determine the:
- DC input power
 - Maximum ac output power
 - The circuit efficiency

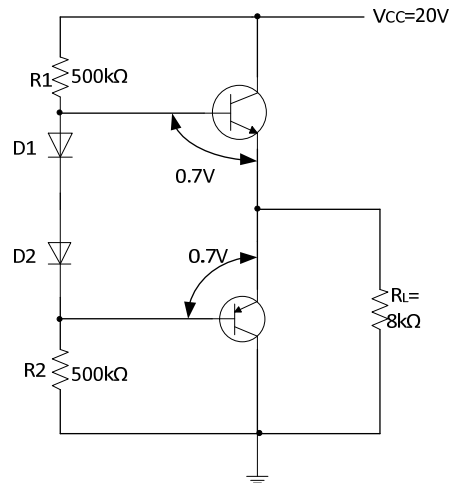


Figure 7

QUESTION FOUR

- a) Explain each of the following operational amplifier characteristics
- Frequency response
 - Slew rate
- (2 marks)**
- b) A 741 op-amp has bias currents $I_{B+} = 0.4\mu A$ and $I_{B-} = 0.3\mu S$. Determine the
- average bias current I_B ;
 - Offset current I_{OS} .
- (4 marks)**
- c) Figure 8 shows an operational amplifier circuit. Show that :
- $$V = 2.3 \frac{kT}{q} \log_{10} \frac{I}{I_0}$$

where I_0 is the theoretical reverse saturation current.
 - $$v_0 = -2.3 \frac{kT}{q} \log_{10} \frac{I}{I_0} \left(\frac{R_1 + R_2}{R_1} \right)$$

d) State TWO applications of logarithmic amplifier

(7 marks)

(2 marks)

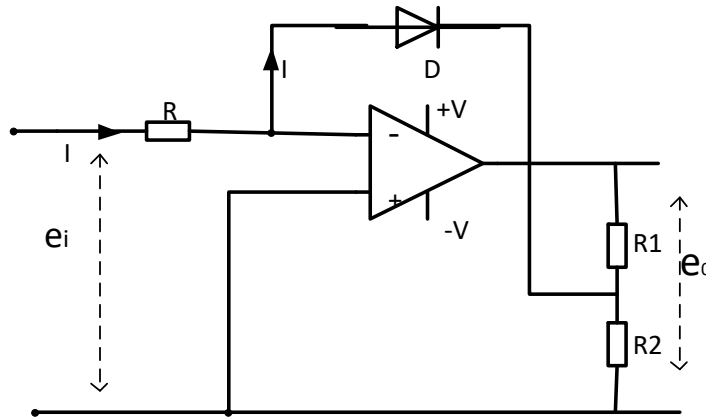


Figure 8

QUESTION 5

a) State **one advantage** and **one disadvantage** of Wien-bridge oscillators

(2 marks)

b) (i) Figure 9 shows a Wien Bridge oscillator. Derive the expressions for the:

- I. Resonant frequency
- II. Feedback gain

(6 marks)

(ii) Design the Wien-bridge in Fig. 8 to oscillate at $f_0 = 800\text{Hz}$. Assume $R = R_1 = 10\text{k}\Omega$

(4 marks)

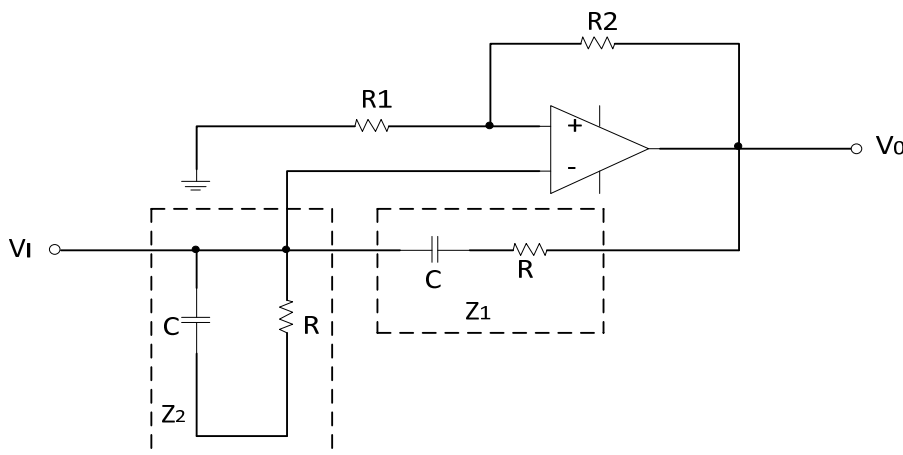


Figure 9

c) Calculate the resonance frequency of a Hartley oscillator with the elements of the tank circuit as $L_1 = 1.5\text{mH}$, $L_2 = 10\text{mH}$ and $C = 470\text{pF}$

(3 marks)